



$$LC\ddot{u}_c(t) + RC\dot{u}_c(t) + u_c(t) = u_r(t)$$

$$\frac{U_c(s)}{U_r(s)} = \frac{1}{LCs^2 + RCs + 1}$$